

This part of the experiment is prepared with Online LaTeX Editor Overleaf. Visit the website for the source here:

<https://www.overleaf.com/read/xymdvxntjkyk#386e99>

1. EXPERIMENT 6 - PRELIMINARY WORK

1.1 Find the roots of the characteristic equation that governs the transient behavior of the voltage shown in *Fig. 1* if $R = 300 \Omega$, $L = 50 \text{ mH}$, and $C = 0.2 \mu\text{F}$. Will the response be overdamped, underdamped, or critically damped? What value of R causes the response to be critically damped?

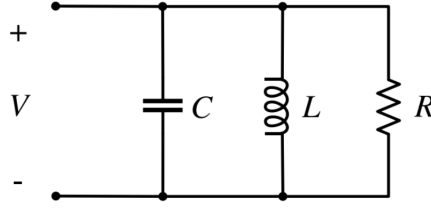


Figure 1

Answer: Let I_R , I_L , and I_C be the currents through the resistor, inductor, and capacitor, respectively, directed downward. By KCL,

$$I_R + I_L + I_C = 0 \implies \frac{V}{R} + \frac{1}{L} \int_0^t V(\tau) d\tau + I_L(0) + C \frac{dV}{dt} = 0.$$

Differentiate each side with respect to t .

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2 V}{dt^2} = 0 \implies \frac{d^2 V}{dt^2} + \frac{1}{RL} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

This is a second-order homogeneous ordinary differential equation with constant coefficients. Therefore, we can extract the characteristic equation.

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \implies s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\frac{1}{4R^2C^2} - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

α is the neper frequency and ω_0 is the resonant frequency.

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 300 \cdot 0.2 \cdot 10^{-6}} = 8333 \frac{\text{rad}}{\text{s}}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \cdot 10^{-3} \cdot 0.2 \cdot 10^{-6}}} = 10^4 \frac{\text{rad}}{\text{s}}$$

Then the roots are

$$s_{1,2} = -8333 \pm \sqrt{8333^2 - 10000^2} = -8333 \pm j 5528.$$

Since we have two distinct complex roots, the response is underdamped.

For the response to be critically damped, set $\alpha = \omega_0$.

$$\alpha = \omega_0 \implies \frac{1}{2RC} = \frac{1}{\sqrt{LC}} \implies R = \frac{\sqrt{LC}}{2C} = \frac{\sqrt{50 \cdot 10^{-3} \cdot 0.2 \cdot 10^{-6}}}{2 \cdot 0.2 \cdot 10^{-6}} = 250 \Omega$$

For critically damped response, $R_{\text{critical}} = 250 \Omega$.

1.2 Suggest a method to observe and measure the current on the inductor in *Fig. 1* using the oscilloscope.

Answer: We may insert a shunt resistor with low resistance in series with the inductor, and then observe the voltage waveform on the oscilloscope. The ratio of the instantaneous resistor voltage and the resistance gives us the current through the inductor. The circuit is slightly modified, but this yields an approximate inductor current.

1.3 No energy is stored in the 100 mH inductor or the 0.4 μF capacitor when the switch in the circuit shown in *Fig. 2* is closed. Find $V_C(t)$ for $t \geq 0$. Will the response be overdamped, underdamped, or critically damped? What value of R causes the response to be critically damped?

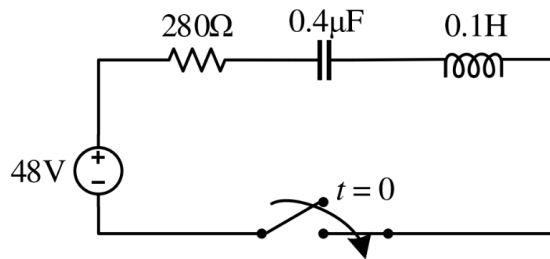


Figure 2

Answer: Let I be the current in the circuit. By KVL,

$$-48 + 280 I + \frac{1}{0.4 \cdot 10^{-6}} \int_0^t I(\tau) d\tau + V_C(0) + 0.1 \frac{dI}{dt} = 0 \quad (1)$$

Differentiate each side with respect to t .

$$280 \frac{dI}{dt} + 25 \cdot 10^5 I + 0.1 \frac{d^2 I}{dt^2} = 0 \implies \frac{d^2 I}{dt^2} + 2800 \frac{dI}{dt} + 25 \cdot 10^6 I = 0$$

This is a second-order homogeneous ordinary differential equation with constant coefficients. Therefore, we can extract the characteristic equation.

$$s^2 + 2800s + 25 \cdot 10^6 = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \implies s_{1,2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} = \frac{280}{2 \cdot 0.1} = 1400 \frac{\text{rad}}{\text{s}}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \cdot 0.4 \cdot 10^{-6}}} = 5000 \frac{\text{rad}}{\text{s}}$$

Then the roots are

$$s_{1,2} = -1400 \pm \sqrt{1400^2 - 5000^2} = -1400 \pm j 4800.$$

Since we have two distinct complex roots, the response is underdamped. The current in the circuit can be expressed as follows.

$$I(t) = e^{-1400t} [c_1 \cos(4800t) + c_2 \sin(4800t)] \quad (2)$$

It is given that no energy is stored in the inductor and capacitor initially. That is,

$$\frac{1}{2} C V_C^2(0) = 0 \implies V_C(0) = 0, \quad \frac{1}{2} L I^2(0^+) = 0 \implies I(0^+) = 0.$$

Therefore,

$$I(0^+) = e^{-1400 \cdot 0} [c_1 \cos(4800 \cdot 0) + c_2 \sin(4800 \cdot 0)] = c_1 = 0.$$

Solve (1) for $\frac{dI}{dt}$.

$$\frac{dI}{dt} = \frac{1}{0.1} \left[48 - \left(\frac{1}{0.4 \cdot 10^{-6}} \int_0^t I(\tau) d\tau + V_C(0) \right) - 280 I \right]$$

At $t = 0$,

$$\left. \frac{dI}{dt} \right|_{t=0} = 480 - 0 - \underbrace{10V_C(0)}_0 - \underbrace{2800 I(0^+)}_0 = 480.$$

Differentiate (2) with respect to t and evaluate the resulting expression at $t = 0$.

$$\begin{aligned} \frac{dI}{dt} &= -1400e^{-1400t} [c_1 \cos(4800t) + c_2 \sin(4800t)] \\ &\quad + e^{-1400t} [-4800c_1 \sin(4800t) + 4800c_2 \cos(4800t)] \\ &= e^{-1400t} [(4800c_2 - 1400c_1) \cos(4800t) + (-1400c_2 - 4800c_1) \sin(4800t)] \end{aligned}$$

$$\left. \frac{dI}{dt} \right|_{t=0} = e^{-1400 \cdot 0} [(4800c_2 - 1400 \cdot 0) \cos(4800 \cdot 0) + (-1400c_2 - 4800 \cdot 0) \sin(4800 \cdot 0)]$$

$$= 4800c_2 = 480 \implies c_2 = \frac{1}{10}$$

The current in the circuit is

$$I(t) = \frac{1}{10} e^{-1400t} \sin(4800t).$$

The voltage across the capacitor is then

$$\begin{aligned} V_C(t) &= \frac{1}{C} \int_0^t I(\tau) d\tau + V_C(0) = \frac{1}{0.4 \cdot 10^{-6}} \int_0^t \frac{1}{10} e^{-1400\tau} \sin(4800\tau) d\tau + 0 \\ &= 25 \cdot 10^4 \int_0^t e^{-1400\tau} \sin(4800\tau) d\tau. \end{aligned}$$

Use integration by parts.

$$\left. \begin{aligned} u &= e^{-1400\tau} \implies du = -1400e^{-1400\tau} d\tau \\ dv &= \sin(4800\tau) d\tau \implies v = -\frac{1}{4800} \cos(4800\tau) \end{aligned} \right\} \implies \int_0^t u dv = uv \Big|_0^t - \int_0^t v du$$

$$V_C(t) = 25 \cdot 10^4 \left(-\frac{1}{4800} e^{-1400\tau} \cos(4800\tau) \Big|_0^t - \frac{1400}{4800} \int_0^t e^{-1400\tau} \cos(4800\tau) d\tau \right)$$

Apply integration by parts once again.

$$\left. \begin{aligned} w &= e^{-1400\tau} \implies dw = -1400e^{-1400\tau} d\tau \\ dz &= \cos(4800\tau) d\tau \implies z = \frac{1}{4800} \sin(4800\tau) \end{aligned} \right\} \implies \int_0^t w dz = wz \Big|_0^t - \int_0^t z dw$$

$$\begin{aligned} V_C(t) &= 25 \cdot 10^4 \left\{ -\frac{e^{-1400\tau}}{4800} \cos(4800\tau) \Big|_0^t - \frac{7}{24} \left[\frac{e^{-1400\tau}}{4800} \sin(4800\tau) \Big|_0^t \right. \right. \\ &\quad \left. \left. - \left(-\frac{1400}{4800} \underbrace{\int_0^t e^{-1400\tau} \sin(4800\tau) d\tau}_{V_C(t)/(25 \cdot 10^4)} \right) \right] \right\} \end{aligned}$$

$$V_C(t) = -e^{-1400t} \left[\frac{625}{12} \cos(4800t) + \frac{4375}{288} \sin(4800t) \right] - \frac{49}{576} V_C(t) + c_3$$

$$V_C(t) = \frac{576}{625} c_3 - e^{-1400t} [48 \cos(4800t) + 14 \sin(4800t)] \text{ V}, \quad t \geq 0$$

We have $V_C(0) = 0$. Therefore,

$$V_C(0) = \frac{576}{625} c_3 - 48 = 0 \implies c_3 = \frac{625}{12}$$

$$\implies \boxed{V_C(t) = 48 - e^{-1400t} [48 \cos(4800t) + 14 \sin(4800t)] \text{ V}, \quad t \geq 0}.$$

For the response to be critically damped, set $\alpha = \omega_0$.

$$\alpha = \omega_0 \implies \frac{R}{2L} = \frac{1}{\sqrt{LC}} \implies R = \frac{2L}{\sqrt{LC}} = \frac{2 \cdot 0.1}{\sqrt{0.1 \cdot 0.4 \cdot 10^{-6}}} = 1000 \, \Omega$$

For critically damped response, $\boxed{R_{\text{critical}} = 1000 \, \Omega}$.