

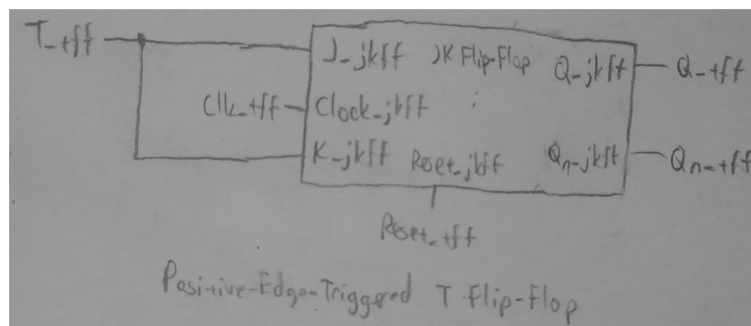
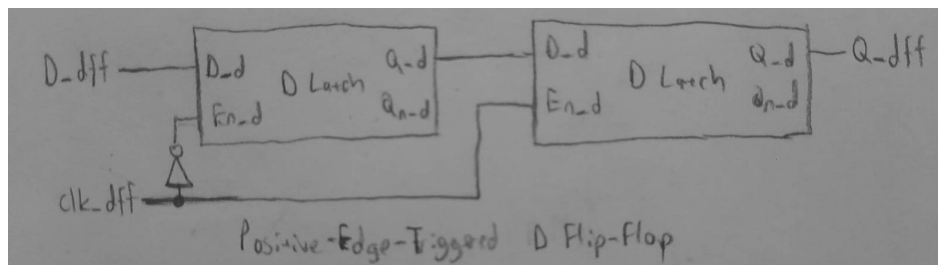
 
 
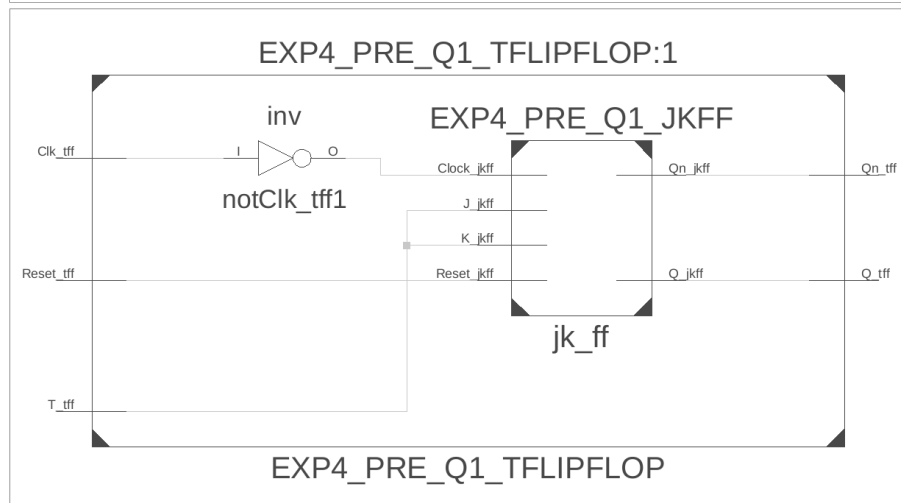
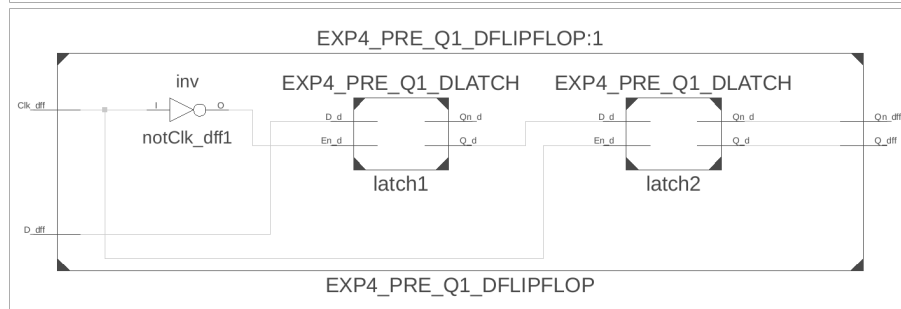


## EXPERIMENT 4 PRELIMINARY WORK

### Q1: 1. Analytical Solution


*Hand-drawn circuits and RTL schematics*

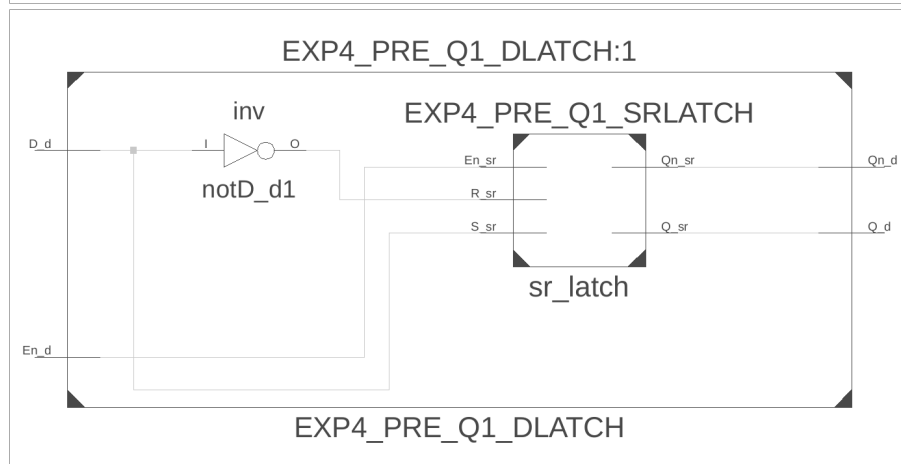

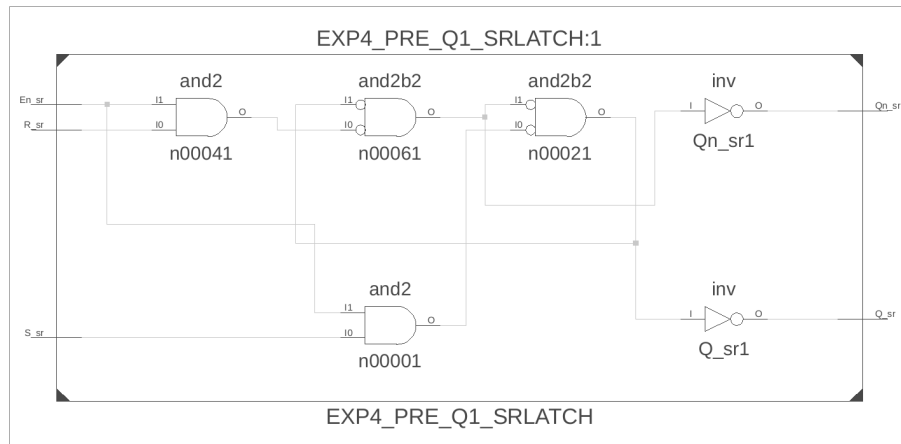


CircuitLab


### a. Sr Latch with NAND Gates

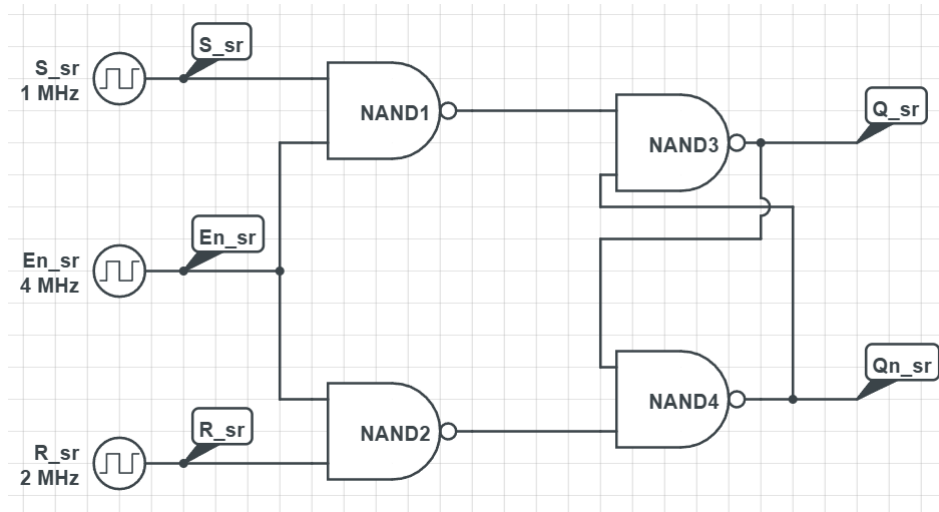


Graph of Input S\_sr

 


Graph of Input En\_sr

 


Graph of Input R\_sr

 


Graph of Output Q\_sr

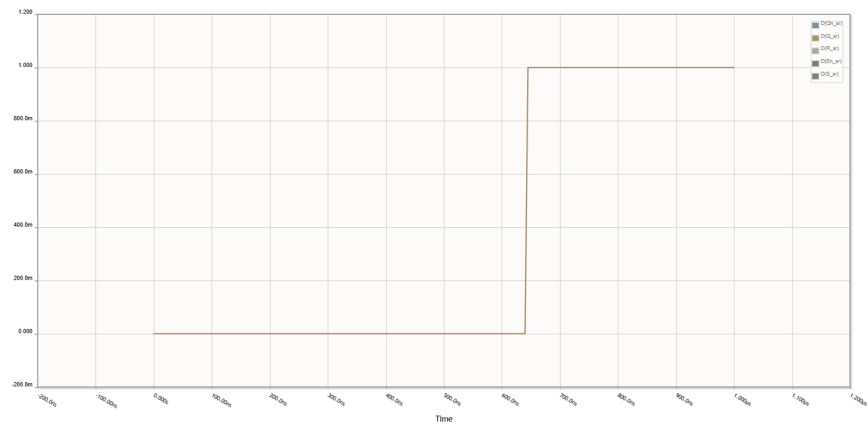


Graph of Output Qn\_sr

 


## b. D Latch

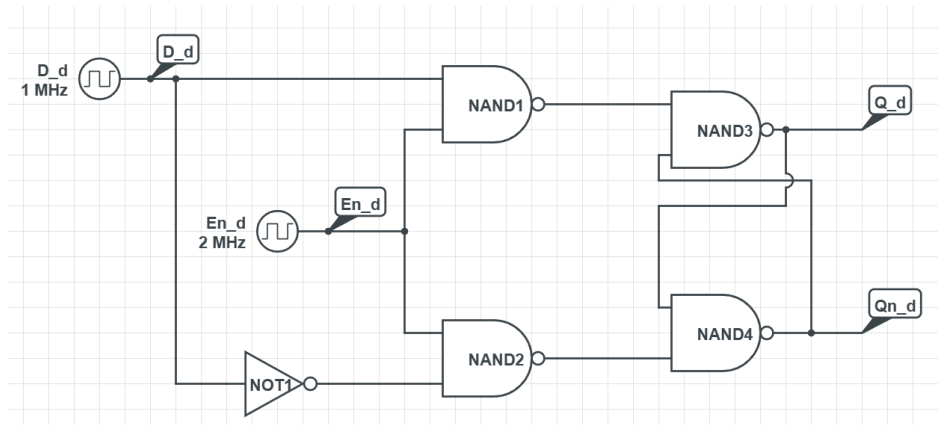


Graph of Input D\_d

 


Graph of Input En\_d

 


Graph of Output Q\_d

 


Graph of Output Qn\_d

 

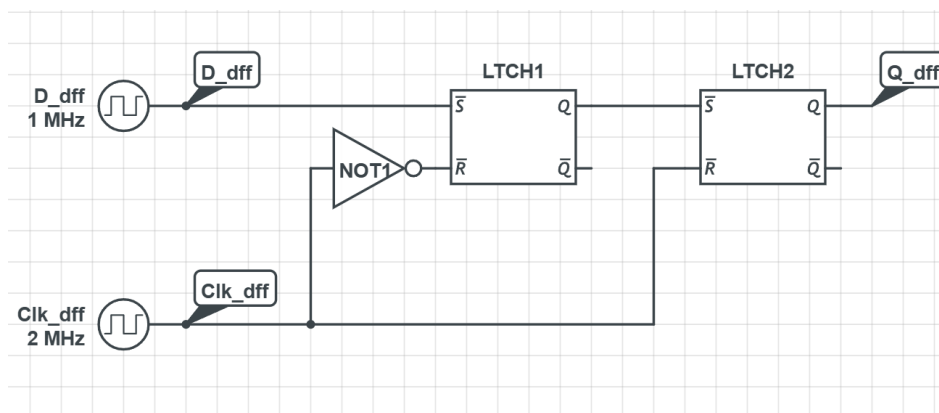
### c. Positive-Edge-Triggered D Flip-Flop




Graph of Input D\_dff

 


Graph of Input Clk\_dff

 


Graph of Output Q\_dff

 


d. Positive-Edge-Triggered T Flip-Flop

 

Graph of Input T\_tff

 


Graph of Input Clk\_tff

 




Graph of Output Q\_tff

 

Graph of Output Qn\_tff

 

## 2. Codes

### *VHDL - a. SR Latch with NAND Gates*

---

```

library ieee;
use ieee.std_logic_1164.all;
entity EXP4_PRE_Q1_SRLATCH is
    port ( S_sr, R_sr, En_sr : in  std_logic; Q_sr, Qn_sr : out std_logic);
end EXP4_PRE_Q1_SRLATCH;
architecture Behavioral of EXP4_PRE_Q1_SRLATCH is
    signal temp_Q, temp_Qn : STD_LOGIC;
begin
    temp_Q <= (S_sr nand En_sr) nand temp_Qn;
    temp_Qn <= (R_sr nand En_sr) nand temp_Q;
    Q_sr <= temp_Q; Qn_sr <= temp_Qn;
end Behavioral;

```

---

*VHDL - b. D Latch*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q1_DLATCH is
    port ( D_d, En_d : in  std_logic; Q_d, Qn_d : out std_logic);
end EXP4_PRE_Q1_DLATCH;
architecture Behavioral of EXP4_PRE_Q1_DLATCH is
    component EXP4_PRE_Q1_SRLATCH
        port ( S_sr, R_sr, En_sr : in  std_logic; Q_sr, Qn_sr : out std_logic);
    end component;
    signal notD_d : std_logic;
begin
    notD_d <= not D_d;
    sr_latch : EXP4_PRE_Q1_SRLATCH port map (D_d, notD_d, En_d, Q_d, Qn_d);
end Behavioral;

```

---

*VHDL - c. Positive-Edge-Triggered D Flip-Flop*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q1_DFLIPFLOP is
    port ( D_dff, Clk_dff : in  std_logic;
          Q_dff, Qn_dff : out std_logic);
end EXP4_PRE_Q1_DFLIPFLOP;
architecture Behavioral of EXP4_PRE_Q1_DFLIPFLOP is
    component EXP4_PRE_Q1_DLATCH
        port ( D_d, En_d : in  std_logic; Q_d, Qn_d : out std_logic);
    end component;
    signal notClk_dff, Q1_dff, Q1n_dff : std_logic;
begin
    notClk_dff <= not Clk_dff;
    latch1 : EXP4_PRE_Q1_DLATCH port map (D_dff, notClk_dff, Q1_dff, Q1n_dff);
    latch2 : EXP4_PRE_Q1_DLATCH port map (Q1_dff, Clk_dff, Q_dff, Qn_dff);
end Behavioral;

```

---

*VHDL - d. JK Flip-Flop with Reset State*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q1_JKFF is
    Port ( J_jkff, K_jkff, Reset_jkff, Clock_jkff : in STD_LOGIC;
          Q_jkff, Qn_jkff : out STD_LOGIC);
end EXP4_PRE_Q1_JKFF;
architecture Behavioral of EXP4_PRE_Q1_JKFF is
    signal tempQ: std_logic;
begin
    process (Reset_jkff, Clock_jkff)

```

```

begin
    if Clock_jkff'event and Clock_jkff = '1' then
        if Reset_jkff = '1' then tempQ <= '0';
            elsif (J_jkff='0' and K_jkff='0') then tempQ <= tempQ;
            elsif (J_jkff='0' and K_jkff='1') then tempQ <= '0';
            elsif (J_jkff='1' and K_jkff='0') then tempQ <= '1';
            elsif (J_jkff='1' and K_jkff='1') then tempQ <= not (tempQ);
        end if;
    end if;
end process;
Q_jkff <= tempQ; Qn_jkff <= not tempQ;
end Behavioral;

```

---

#### *VHDL - d. Positive-Edge-Triggered T Flip-Flop*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q1_TFLIPFLOP is
    Port ( T_tff, Reset_tff, Clk_tff : in std_logic;
           Q_tff, Qn_tff : out std_logic);
end EXP4_PRE_Q1_TFLIPFLOP;
architecture Behavioral of EXP4_PRE_Q1_TFLIPFLOP is
    component EXP4_PRE_Q1_JKFF
        Port ( J_jkff, K_jkff, Reset_jkff, Clock_jkff : in STD_LOGIC;
              Q_jkff, Qn_jkff : out STD_LOGIC);
    end component;
    signal notClk_tff : std_logic;
begin
    jkff : EXP4_PRE_Q1_JKFF port map(T_tff, T_tff, Reset_tff,
                                     Clk_tff, Q_tff, Qn_tff);
end Behavioral;

```

---

### 3. Results

#### *Test bench - a. SR Latch with NAND Gates*


---

```

stim_proc: process
begin
    En_sr <= '0'; S_sr <= '0'; R_sr <= '0'; wait for 100 ns;
    En_sr <= '0'; S_sr <= '0'; R_sr <= '1'; wait for 100 ns;
    En_sr <= '0'; S_sr <= '1'; R_sr <= '0'; wait for 100 ns;
    En_sr <= '0'; S_sr <= '1'; R_sr <= '1'; wait for 100 ns;
    En_sr <= '1'; S_sr <= '0'; R_sr <= '0'; wait for 100 ns;
    En_sr <= '1'; S_sr <= '0'; R_sr <= '1'; wait for 100 ns;
    En_sr <= '1'; S_sr <= '1'; R_sr <= '0'; wait for 100 ns;
    En_sr <= '1'; S_sr <= '1'; R_sr <= '1'; wait for 100 ns;
end process;


```

---

 

 
### Test bench - b. D Latch

```
stim_proc: process
begin
    En_d <= '0'; D_d <= '0'; wait for 100 ns;
    En_d <= '0'; D_d <= '1'; wait for 100 ns;
    En_d <= '1'; D_d <= '0'; wait for 100 ns;
    En_d <= '1'; D_d <= '1'; wait for 100 ns;
end process;
```



 
### Test bench - c. Positive-Edge-Triggered D Flip-Flop

```
stim_proc: process
begin
    D_dff <= '0'; wait for Clk_dff_period*2;
    D_dff <= '1'; wait for Clk_dff_period*2;
    D_dff <= '0'; wait for Clk_dff_period*2;
    D_dff <= '1'; wait for Clk_dff_period*2;
end process;
```


 
### Test bench - d. Positive-Edge-Triggered T Flip-Flop

```
stim_proc: process
begin
    Reset_tff <= '1'; T_tff <= '0'; wait for Clk_tff_period*2;
    Reset_tff <= '0'; T_tff <= '0'; wait for Clk_tff_period*2;
    T_tff <= '1'; wait for Clk_tff_period*2;
    T_tff <= '0'; wait for Clk_tff_period*2;
end process;
```



## Q2: 1. Analytical Solution

Present State		Input	Next State		Output
D1(t)	D2(t)	x	D1(t+1)	D2(t+1)	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	0	1	1

State Table for Mealy Sequence Detector

$$y = D1(t) D2(t) x$$

x	D1(t) D2(t)			
	00	01	11	10
0	0	1	1	0
1	0	0	0	1


$$D1(t+1) = x' D2(t) + x D1(t) D2'(t)$$


x	D1(t) D2(t)			
	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$D2(t+1) = x$$

The characteristic equation of a D flip-flop is  $D = Q(t+1)$ . Therefore, we may use 2 D flip-flops for  $D1(t+1)$  and  $D2(t+1)$  and treat the next states as the inputs of the D flip-flops.

Hand-drawn circuit and RTL schematic

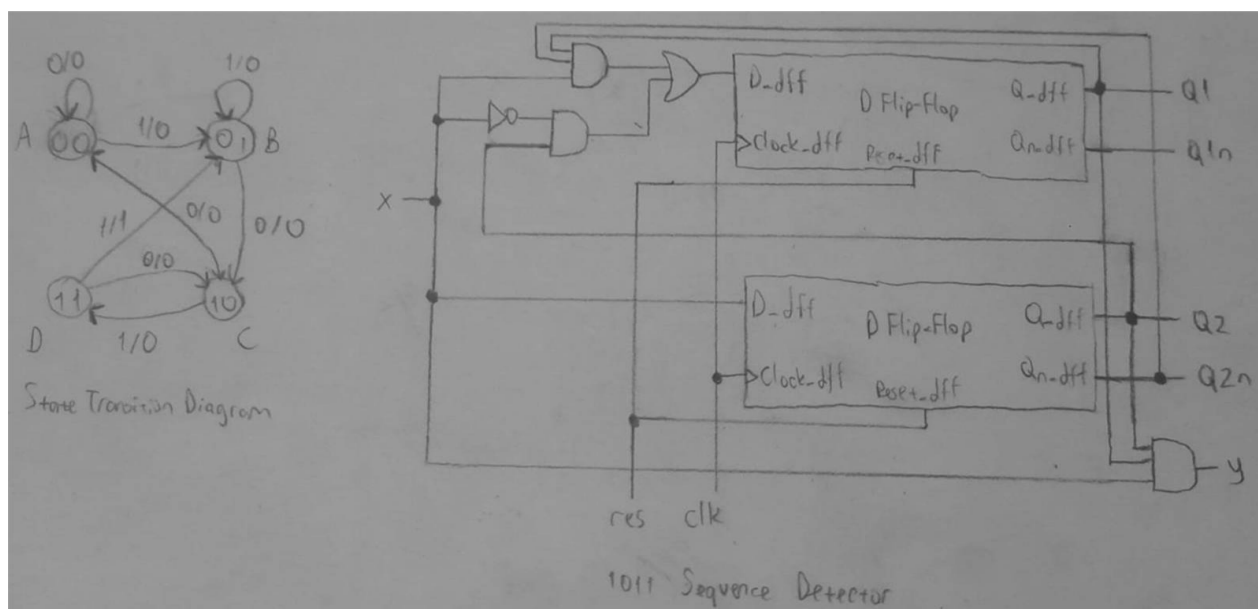

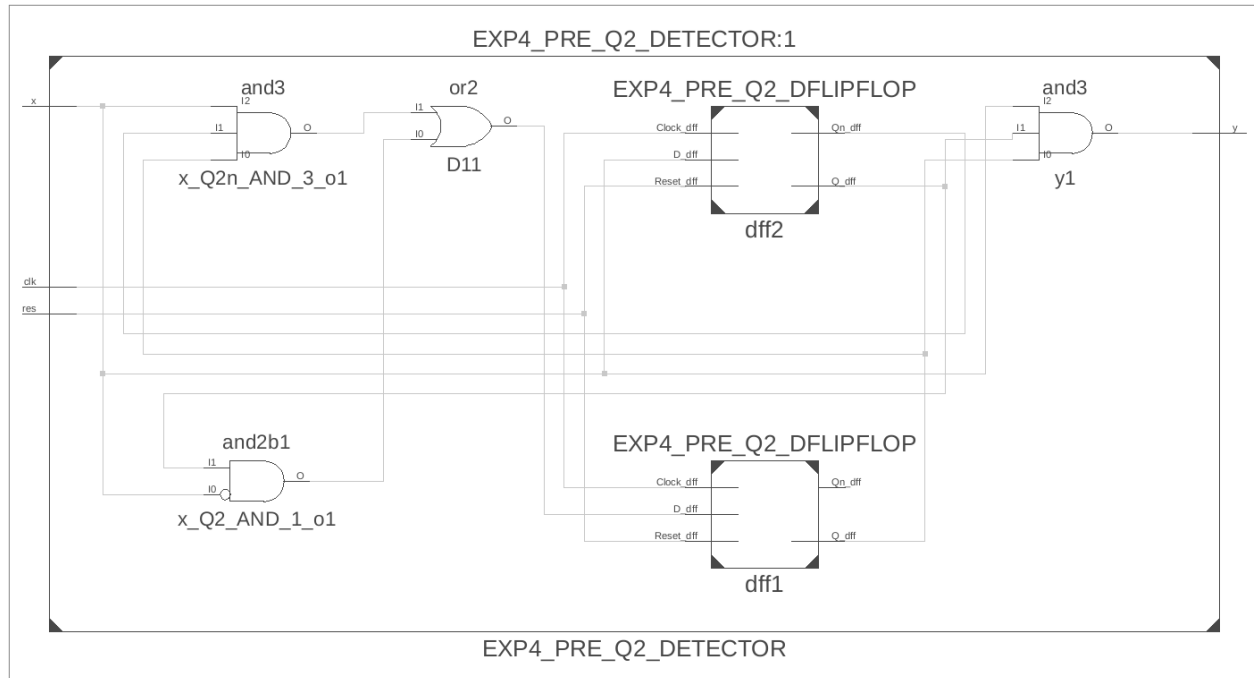

## 2. Codes

### VHDL - D Flip-Flop

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity EXP4_PRE_Q2_DFLIPFLOP is
    Port ( D_dff, Reset_dff, Clock_dff : in STD_LOGIC;
          Q_dff, Qn_dff : out STD_LOGIC);
end EXP4_PRE_Q2_DFLIPFLOP;

architecture Behavioral of EXP4_PRE_Q2_DFLIPFLOP is
    signal tempQ : STD_LOGIC;
begin
    process (Reset_dff, Clock_dff)
    begin
        if Clock_dff'event and Clock_dff = '1' then
            if Reset_dff = '1' then tempQ <= '0';
            else tempQ <= D_dff;
            end if;
        end if;
    end process;
    Q_dff <= tempQ;
    Qn_dff <= not tempQ;
end Behavioral;

```

*VHDL - Detector*


---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity EXP4_PRE_Q2_DETECTOR is
    Port ( x, res, clk : in STD_LOGIC;
          y : out STD_LOGIC);
end EXP4_PRE_Q2_DETECTOR;

architecture Behavioral of EXP4_PRE_Q2_DETECTOR is
    component EXP4_PRE_Q2_DFLIPFLOP
        Port ( D_dff, Reset_dff, Clock_dff : in STD_LOGIC;
              Q_dff, Qn_dff : out STD_LOGIC);
    end component;
    signal D1, D2, Q1, Q1n, Q2, Q2n : STD_LOGIC;
begin
    D1 <= (not x and Q2) or (x and Q1 and Q2n) ;
    D2 <= x;
    dff1 : EXP4_PRE_Q2_DFLIPFLOP port map(D1, res, clk, Q1, Q1n);
    dff2 : EXP4_PRE_Q2_DFLIPFLOP port map(D2, res, clk, Q2, Q2n);
    y <= Q1 and Q2 and x;
end Behavioral;

```

---

**3. Results***Test bench*

 

---

```

stim_proc: process
begin
    res <= '1'; wait for clk_period;
    x <= '0'; res <= '0'; wait for clk_period;
    x <= '1'; wait for clk_period;
    x <= '1'; wait for clk_period;
    x <= '0'; wait for clk_period;
    x <= '0'; wait for clk_period;
    x <= '1'; wait for clk_period;
    x <= '0'; wait for clk_period;
    x <= '1'; wait for clk_period;
    x <= '1'; wait for clk_period;
    x <= '1'; wait for clk_period;
    x <= '0'; wait for clk_period;
end process;

```

---



**Q3: 1. Analytical Solution**

Present State	Input		Next State	Output
T(t)	Data	parityin	T(t + 1)	paritychk
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

State Table for Parity Generator &amp; Checker

T(t)	Data parityin			
	00	01	11	10
0	0	0	1	1
1	0	0	1	1


$$T(t+1) = \text{Data}$$

T(t)	Data parityin			
	00	01	11	10
0	1	0	0	1
1	0	1	1	0


$$\text{paritychk} = T'(t) \text{ parityin}' + T(t) \text{ parityin}$$

$$\text{paritychk} = (T(t) \oplus \text{parityin})'$$

Hand-drawn circuit and RTL schematic

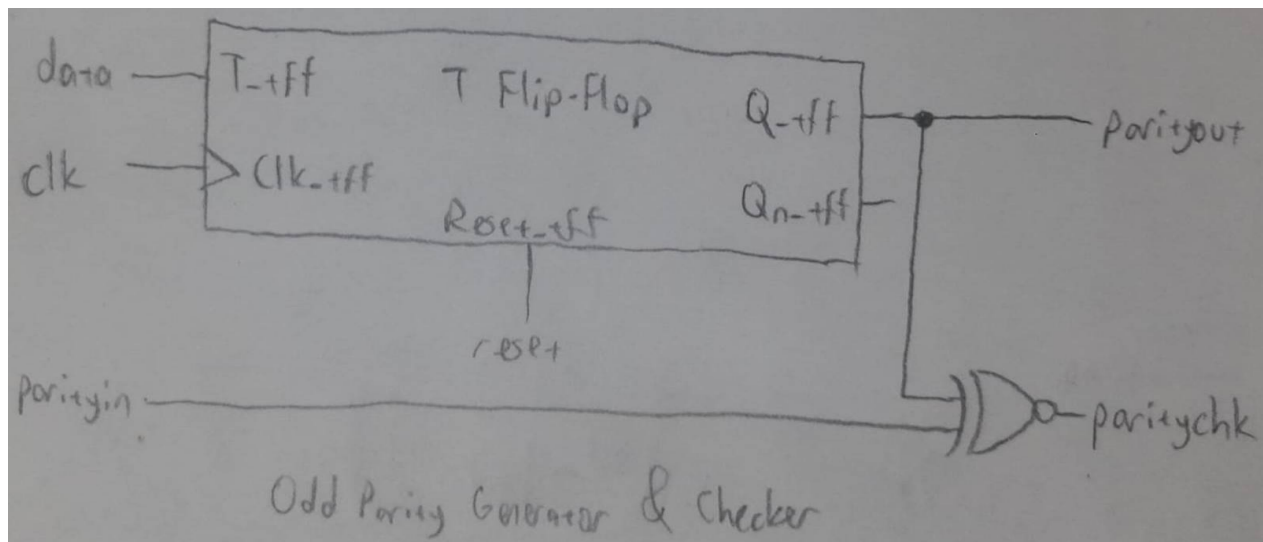



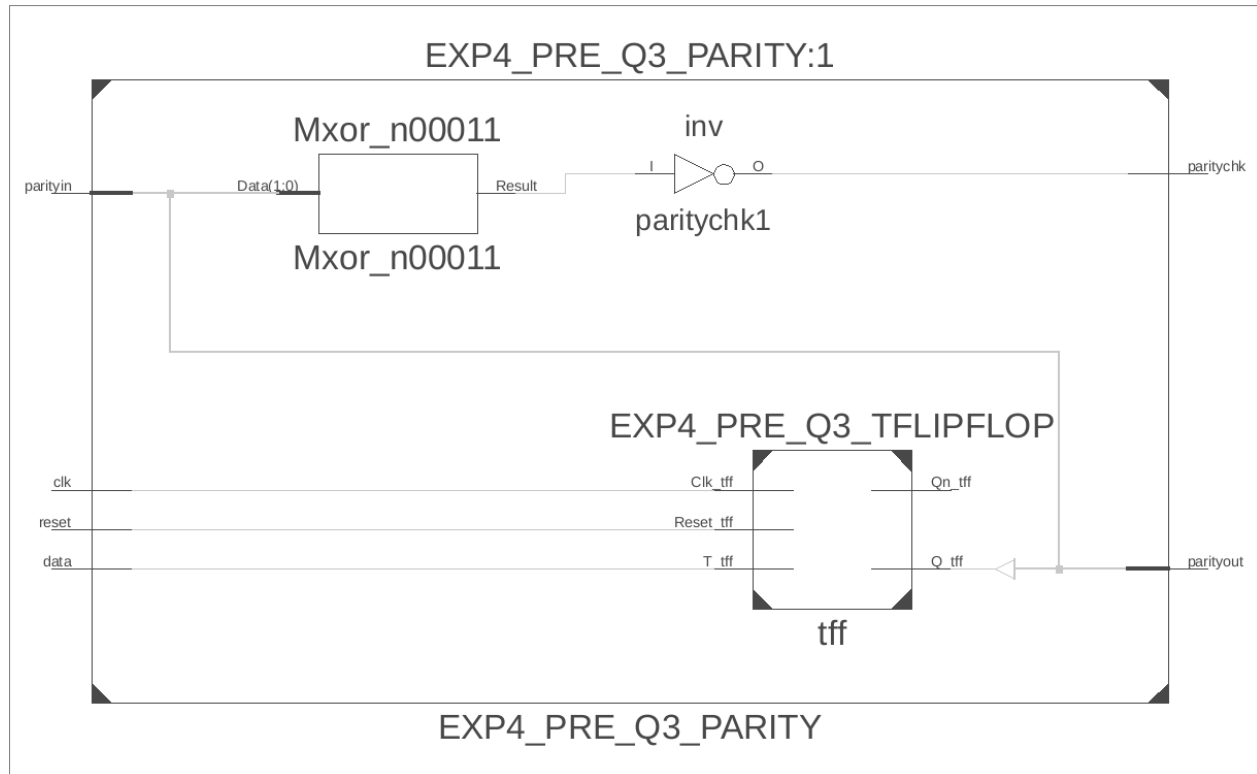

## 2. Codes

### VHDL - T Flip-Flop

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q3_TFLIPFLOP is
    port ( T_tff, Reset_tff, Clk_tff : in std_logic;
          Q_tff, Qn_tff : out std_logic);
end EXP4_PRE_Q3_TFLIPFLOP;
architecture Behavioral of EXP4_PRE_Q3_TFLIPFLOP is
    signal tempQ : std_logic;
begin
    process (Reset_tff, Clk_tff)
    begin
        if Clk_tff'event and Clk_tff = '1' then
            if Reset_tff = '1' then tempQ <= '0';
            elsif T_tff = '1' then tempQ <= not tempQ;
            end if;
        end if;
    end process;
    Q_tff <= tempQ; Qn_tff <= not tempQ;
end Behavioral;

```

*VHDL - Parity Generator & Checker*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity EXP4_PRE_Q3_PARITY is
    Port ( data, parityin, reset, clk : in STD_LOGIC;
          parityout, paritychk : out STD_LOGIC);
end EXP4_PRE_Q3_PARITY;

architecture Behavioral of EXP4_PRE_Q3_PARITY is

    component EXP4_PRE_Q3_TFLIPFLOP
        port ( T_tff, Reset_tff, Clk_tff : in std_logic;
              Q_tff, Qn_tff : out std_logic);
    end component;

    signal tempQ, tempQn: STD_LOGIC;

begin
    tff : EXP4_PRE_Q3_TFLIPFLOP port map (data, reset, clk, tempQ, tempQn);
    parityout <= tempQ;
    paritychk <= tempQ xnor parityin;
end Behavioral;

```

---

**3. Results***Test bench*

---

```

stim_proc: process
begin
    -- Data 1
    reset <= '1'; parityin <= '1'; wait for clk_period;
    reset <= '0'; data <= '1'; wait for clk_period;
    data <= '0'; wait for clk_period;
    data <= '1'; wait for clk_period;
    data <= '1'; wait for clk_period;
    data <= '0'; wait for clk_period;
    data <= '1'; wait for clk_period;
    data <= '0'; wait for clk_period;
    data <= '1'; wait for clk_period;
    data <= '1'; wait for clk_period;
    data <= '0'; wait for clk_period;

```


```
-- Data 2
reset <= '1'; parityin <= '1'; wait for clk_period;
reset <= '0'; data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '1'; wait for clk_period;

-- Data 3
reset <= '1'; parityin <= '0'; wait for clk_period;
reset <= '0'; data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '0'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '0'; wait for clk_period;


-- Data 4
reset <= '1'; parityin <= '0'; wait for clk_period;
reset <= '0'; data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
data <= '1'; wait for clk_period;
end process;
```

---


*Data 1*

 


*Data 2*

 

*Data 3*

 

*Data 4*

 

**Q4: 1. Analytical Solution**



J	K	Q(t)	Q(t+1)	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

JK				
	00	01	11	10
Q				
0	0	0	1	1
1	1	0	0	1

$$D = QK' + Q'J$$

Truth Table for D Flip-Flop  
Excitation Table for JK Flip-Flop

*Hand-drawn circuit and RTL schematic*

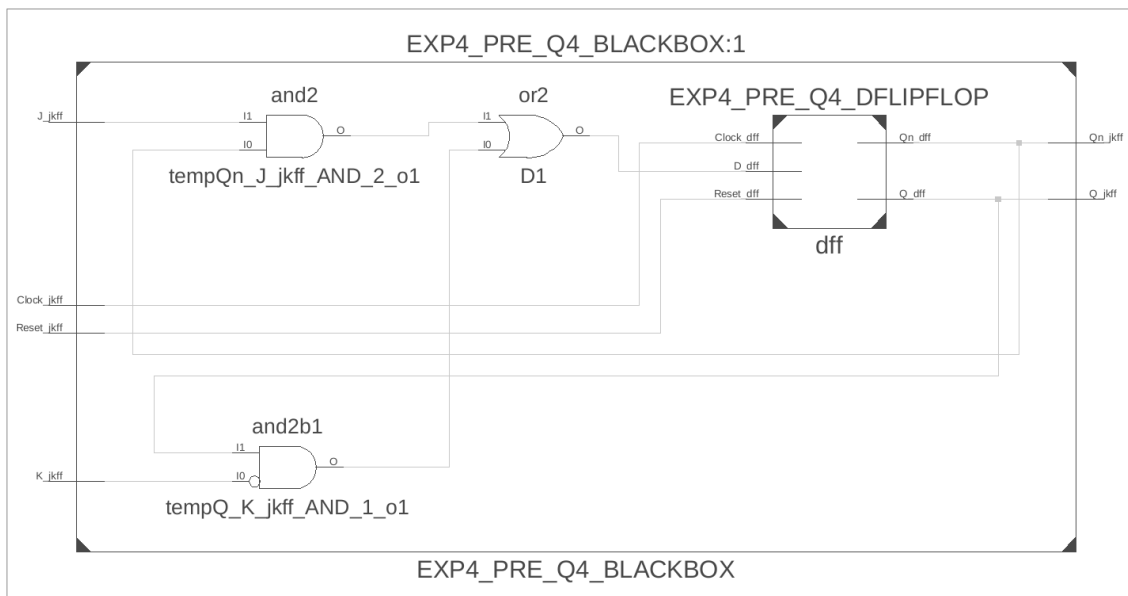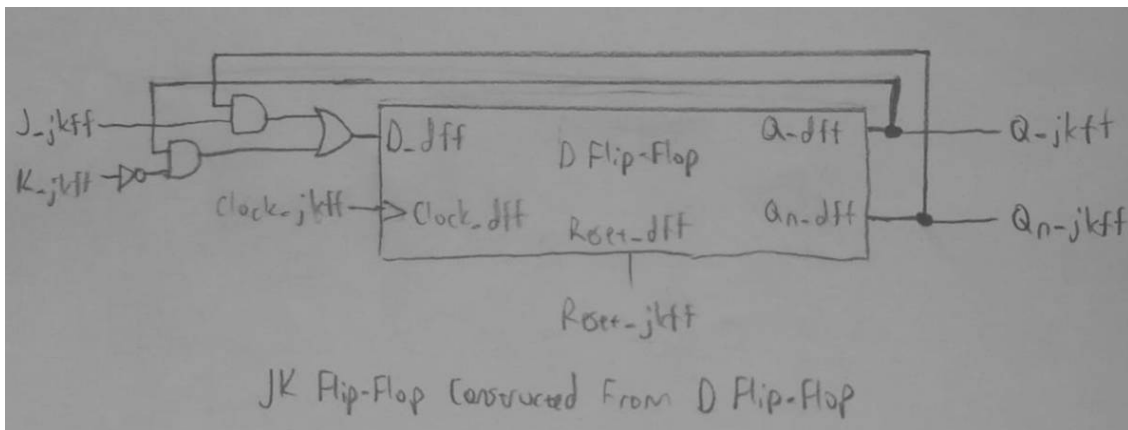

## 2. Codes

### *VHDL - D Flip-Flop*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q4_DFLIPFLOP is
    Port ( D_dff, Reset_dff, Clock_dff : in STD_LOGIC;
          Q_dff, Qn_dff : out STD_LOGIC);
end EXP4_PRE_Q4_DFLIPFLOP;

architecture Behavioral of EXP4_PRE_Q4_DFLIPFLOP is
    signal tempQ : STD_LOGIC;
begin
    process (Reset_dff, Clock_dff)
    begin
        if Clock_dff'event and Clock_dff = '1' then
            if Reset_dff = '1' then tempQ <= '0';
            else tempQ <= D_dff;
            end if;
        end if;
    end process;
    Q_dff <= tempQ; Qn_dff <= not tempQ;
end Behavioral;

```

---

### *VHDL - Blackbox*

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity EXP4_PRE_Q4_BLACKBOX is
    Port ( J_jkff, K_jkff, Reset_jkff, Clock_jkff : in STD_LOGIC;
          Q_jkff, Qn_jkff : out STD_LOGIC);
end EXP4_PRE_Q4_BLACKBOX;

architecture Behavioral of EXP4_PRE_Q4_BLACKBOX is
    component EXP4_PRE_Q4_DFLIPFLOP
        Port ( D_dff, Reset_dff, Clock_dff : in STD_LOGIC;
              Q_dff, Qn_dff : out STD_LOGIC);
    end component;
    signal tempQ, tempQn, D : STD_LOGIC;
begin
    D <= (tempQ and not K_jkff) or (tempQn and J_jkff);
    dff : EXP4_PRE_Q4_DFLIPFLOP port map (D, Reset_jkff, Clock_jkff,
                                          tempQ, tempQn);

    Q_jkff <= tempQ;
    Qn_jkff <= tempQn;
end Behavioral;

```

---

### 3. Results

#### *Test bench*

```
stim_proc: process
begin
  Reset_jkff <= '1'; wait for Clock_jkff_period;
  J_jkff <= '0'; K_jkff <= '0'; Reset_jkff<='0'; wait for Clock_jkff_period;
  J_jkff <= '0'; K_jkff <= '1'; wait for Clock_jkff_period;
  J_jkff <= '1'; K_jkff <= '0'; wait for Clock_jkff_period;
  J_jkff <= '1'; K_jkff <= '1'; wait for Clock_jkff_period*2;
  J_jkff <= '0'; K_jkff <= '1'; wait for Clock_jkff_period;
  J_jkff <= '0'; K_jkff <= '0'; wait for Clock_jkff_period;
end process;
```

