

This part of the experiment is prepared with Online LaTeX Editor Overleaf. Visit the website for the source here:

<https://www.overleaf.com/read/xqcznrxycrxx#b840fb>

1. EXPERIMENT 5 - PRELIMINARY WORK

1.1 For the circuit given in *Fig. 1*, sketch roughly the waveforms of $V_C(t)$ and $V_R(t)$.

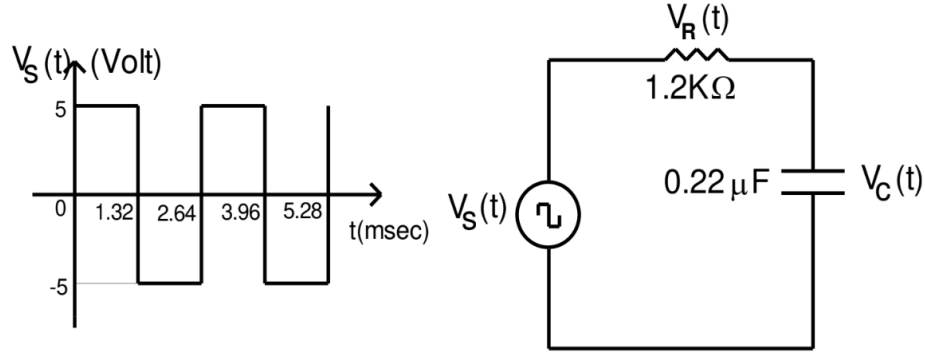


Figure 1

Answer: By a KCL equation for $0 < t < 1.32$ ms,

$$\begin{aligned} \frac{V_C - V_S}{R} &= C \frac{dV_C}{dt} \implies \frac{dV_C}{dt} = \frac{V_C - V_S}{RC} \implies \frac{dV_C}{V_C - V_S} = \frac{dt}{RC} \\ \implies \int_{V_C(0)}^{V_C(t)} \frac{dx}{x - V_S} &= \int_0^t \frac{d\tau}{RC} \implies -\ln|x - V_S| \Big|_{x=V_C(0)}^{x=V_C(t)} = \frac{125000}{33} \tau \Big|_{\tau=0}^{\tau=t} \\ \implies \ln \left(\frac{V_C(t) - V_S}{V_C(0) - V_S} \right) &= -\frac{125000t}{33} \implies V_C(t) = V_S + (V_C(0) - V_S)e^{-125000t/33} \end{aligned}$$

The voltage across the resistor is then

$$V_R = V_S - V_C \implies V_R = (V_S - V_C(0))e^{-125000t/33}$$

One problem is that we need to know the value of $V_C(0)$, which is not given in the question. Assume that $V_C(0) = -5$ V. The voltages across the elements are

$$\left. \begin{aligned} V_C(t) &= 5 - 10e^{-125000t/33} \text{ V} \\ V_R(t) &= 10e^{-125000t/33} \text{ V} \end{aligned} \right\} 0 < t < 1.32 \text{ ms}$$

For $1.32 \text{ ms} < t < 2.64 \text{ ms}$, the polarity of the source changes. Assume that the final voltages are attained, i.e., the difference in the voltage at $t = 1.32$ ms and the final voltage is negligible. Therefore, the equations also change sign.

$$\left. \begin{aligned} V_C(t) &= -5 + 10e^{-125000(t-1.32 \text{ ms})/3} \text{ V} \\ V_R(t) &= -10e^{-125000(t-1.32 \text{ ms})/3} \text{ V} \end{aligned} \right\} 1.32 \text{ ms} < t < 2.64 \text{ ms}$$

Since $0 < t < 2.64 \text{ ms}$ comprises one square wave, we can sketch the entire graph.

