

EXPERIMENT 1 PRELIMINARY WORK

Q1: Read the remainders in the backward direction and add the necessary zeros to the left.

$$\begin{array}{lcl}
 \text{a.} & \begin{array}{c|c} 41 & \\ 20 & 1 \\ 10 & 0 \\ 5 & 0 \\ 2 & 1 \\ 1 & 0 \\ 0 & 1 \end{array} & \Rightarrow \boxed{(41)_{10} = (00101001)_2}
 \end{array}
 \quad \parallel \quad
 \begin{array}{lcl}
 \text{b.} & \begin{array}{c|c} 79 & \\ 39 & 1 \\ 19 & 1 \\ 9 & 1 \\ 4 & 1 \\ 2 & 0 \\ 1 & 0 \\ 0 & 1 \end{array} & \Rightarrow \boxed{(79)_{10} = (01001111)_2}
 \end{array}$$



$$\begin{array}{lcl}
 \text{c.} & \begin{array}{c|c} 108 & \\ 54 & 0 \\ 27 & 0 \\ 13 & 1 \\ 6 & 1 \\ 3 & 0 \\ 1 & 1 \\ 0 & 1 \end{array} & \Rightarrow \boxed{(108)_{10} = (01101100)_2}
 \end{array}
 \quad \parallel \quad
 \begin{array}{lcl}
 \text{d.} & \begin{array}{c|c} 127 & \\ 63 & 1 \\ 31 & 1 \\ 15 & 1 \\ 7 & 1 \\ 3 & 1 \\ 1 & 1 \\ 0 & 1 \end{array} & \Rightarrow \boxed{(127)_{10} = (01111111)_2}
 \end{array}$$

$$\begin{array}{lcl}
 \text{e.} & \begin{array}{c|c} 240 & \\ 120 & 0 \\ 60 & 0 \\ 30 & 0 \\ 15 & 0 \\ 7 & 1 \\ 3 & 1 \\ 1 & 1 \\ 0 & 1 \end{array} & \Rightarrow \boxed{(240)_{10} = (11110000)_2}
 \end{array}$$

Q2:

	Decimal form	Hexadecimal form
a. 01001010	$2^6 + 2^3 + 2^1 = \boxed{74}$	$\underbrace{0100}_4 \underbrace{1010}_A = \boxed{4A}$
b. 01110101	$2^6 + 2^5 + 2^4 + 2^2 + 2^0 = \boxed{117}$	$\underbrace{0111}_7 \underbrace{0101}_5 = \boxed{75}$
c. 11110010	$2^7 + 2^6 + 2^5 + 2^4 + 2^1 = \boxed{242}$	$\underbrace{1111}_F \underbrace{0010}_2 = \boxed{F2}$
d. 00101110	$2^5 + 2^3 + 2^2 + 2^1 = \boxed{46}$	$\underbrace{0010}_2 \underbrace{1110}_E = \boxed{2E}$
e. 11010000	$2^7 + 2^6 + 2^4 = \boxed{208}$	$\underbrace{1101}_D \underbrace{0000}_0 = \boxed{D0}$

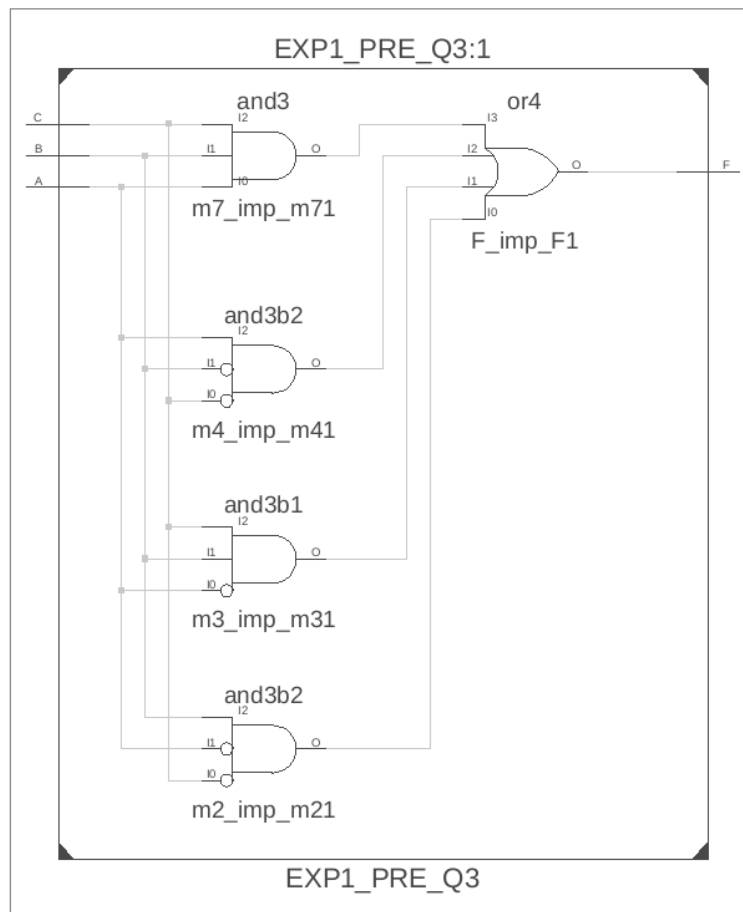 Q3: a. *Hand-drawn circuit and RTL schematic:*



VHDL:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity EXP1_PRE_Q3 is
Port ( A, B, C : in  STD_LOGIC;
      F       : out STD_LOGIC);
end EXP1_PRE_Q3;

architecture Behavioral of EXP1_PRE_Q3 is
    signal m2, m3, m4, m7 : STD_LOGIC;

begin
    m2 <= not A and B and not C;
    m3 <= not A and B and C;
    m4 <= A and not B and not C;
    m7 <= A and B and C;

    F <= m2 or m3 or m4 or m7;
end Behavioral;


```

b. Test bench

```

stim_proc: process
begin
    wait for 100 ns;
    A <= '0'; B <= '1'; C <= '0';
    wait for 100 ns;
    A <= '1'; B <= '1'; C <= '0';
    wait for 100 ns;
    A <= '1'; B <= '0'; C <= '0';
    wait for 100 ns;
    A <= '1'; B <= '0'; C <= '1';
    wait;
end process;

```

 

Q4: a.

x	y	z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

$$\Rightarrow \text{Collect the minterms} \Rightarrow \begin{aligned} A &= x'yz + xy'z + xyz' + xyz \\ B &= x'y'z + x'yz' + xy'z' + xyz \\ C &= x'y'z' + x'yz' + xy'z' + xyz' \end{aligned}$$

b.

$$A: \begin{array}{c|cccc} x \backslash yz & 00 & 01 & 11 & 10 \\ \hline 0 & 0 & 0 & 1 & 0 \\ 1 & 1 & 0 & 1 & 1 \end{array},$$


$$B: \begin{array}{c|cccc} x \backslash yz & 00 & 01 & 11 & 10 \\ \hline 0 & 0 & 1 & 0 & 1 \\ 1 & 1 & 0 & 1 & 0 \end{array},$$


$$C: \begin{array}{c|cccc} x \backslash yz & 00 & 01 & 11 & 10 \\ \hline 0 & 1 & 0 & 0 & 1 \\ 1 & 1 & 0 & 0 & 1 \end{array}$$

$$A = xz + yz + xy,$$

$$B = x \oplus y \oplus z,$$

$$C = z'$$

 c. Hand-drawn circuit and RTL schematic:

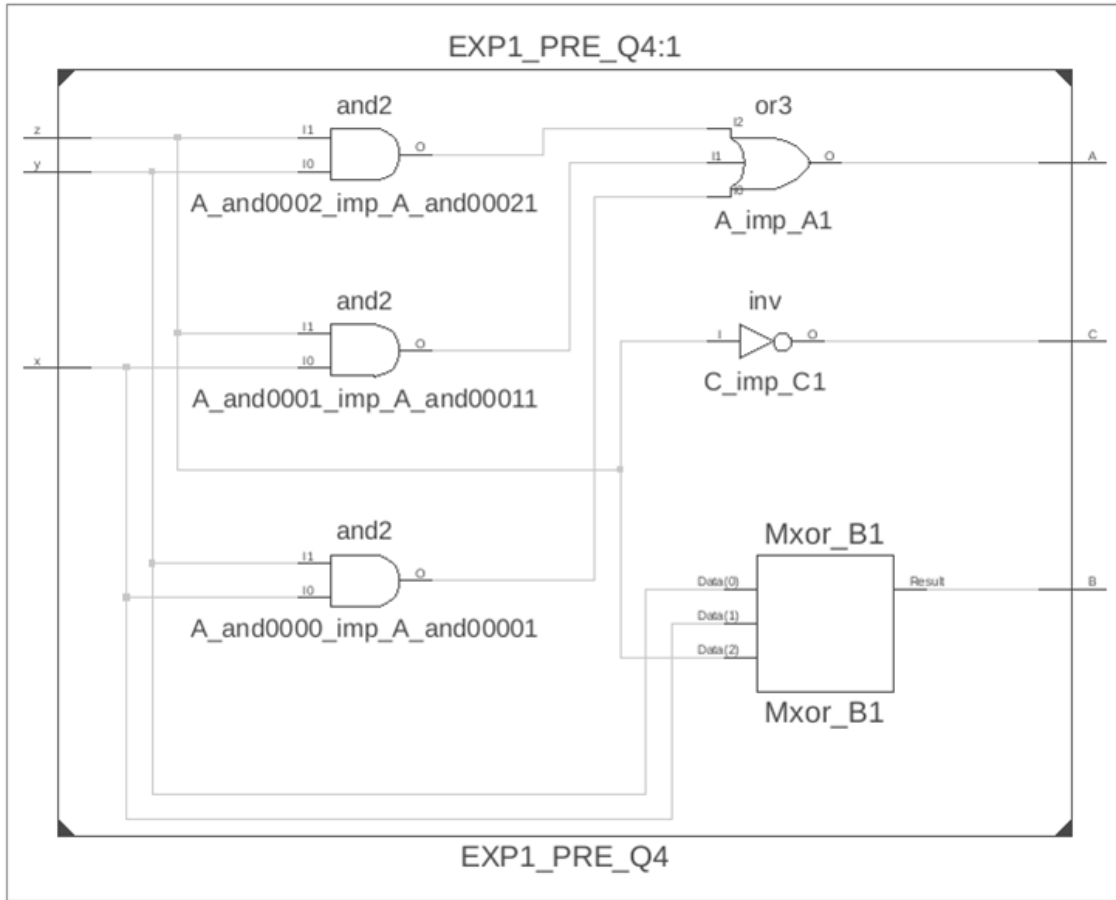

VHDL:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity EXP1_PRE_Q4 is
    Port ( x, y, z : in  STD_LOGIC;
          A, B, C : out STD_LOGIC);
end EXP1_PRE_Q4;

architecture Behavioral of EXP1_PRE_Q4 is

begin
    A <= (x and y) or (x and z) or (y and z);
    B <= x xor y xor z;
    C <= not z;
end Behavioral;
```

d. Test bench

```

stim_proc: process
begin
    wait for 100 ns;
    x <= '0'; y <= '1'; z <= '0';
    wait for 100 ns;
    x <= '1'; y <= '1'; z <= '0';
    wait for 100 ns;
    x <= '1'; y <= '0'; z <= '0';
    wait for 100 ns;
    x <= '1'; y <= '0'; z <= '1';
    wait;
end process;

```

