

This part of the experiment is prepared with Online LaTeX Editor Overleaf and the circuits are drawn in LTspice. Visit the website for the source here:

<https://www.overleaf.com/read/qgkyrtmrpqkd#2fdec2>

3. EXPERIMENT 1 - PRELIMINARY WORK

3.1 Calculate the values of the currents I , I_1 , I_2 , I_3 and I_4 and the voltages V_1 , V_2 , V_3 , V_4 and V_5 in *Figure 6*. Show the meter connections for these measurements.


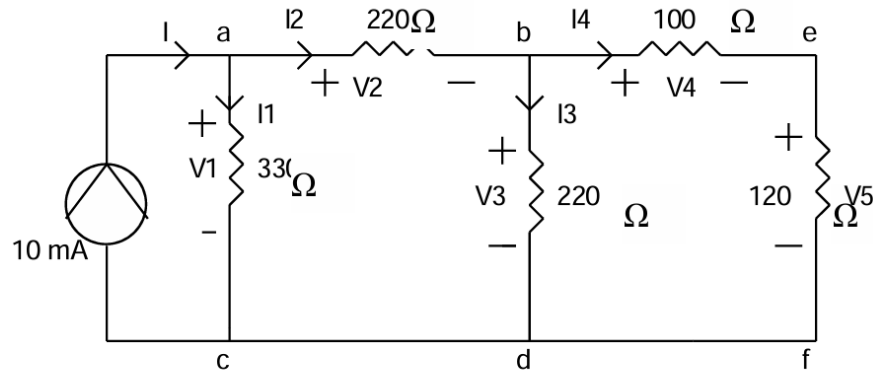


Figure 6.

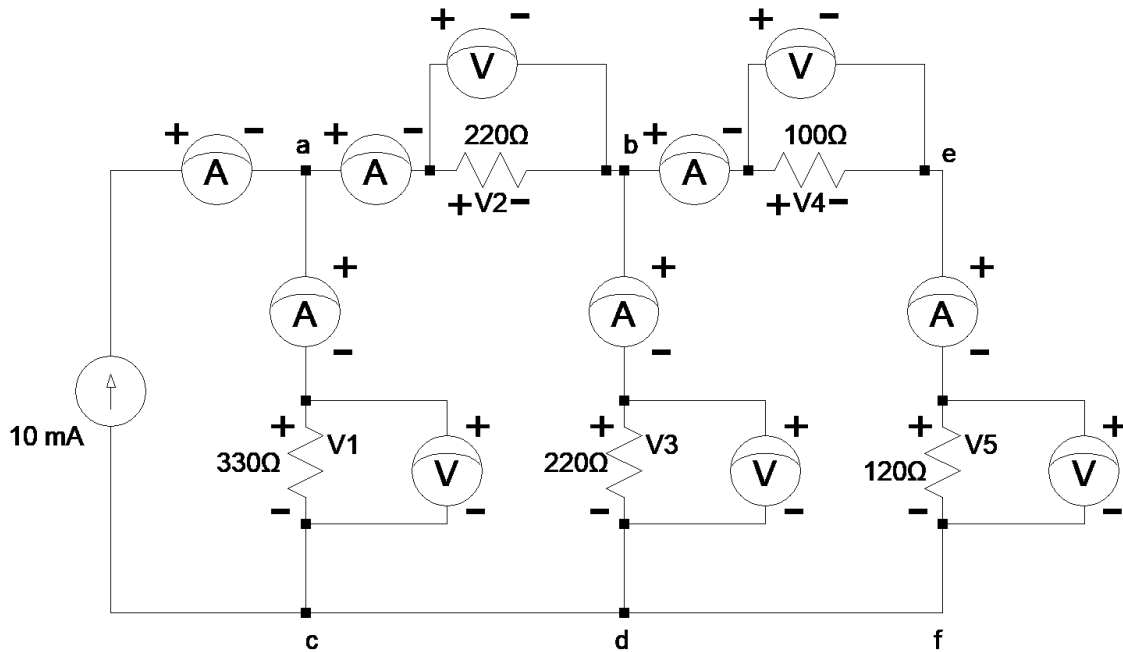Answer: The connections of meters should be as follows.



The ammeters are connected properly so the current enters from the positive side. As for the type of connection, the ammeters are connected in series. Meanwhile, the voltmeters are connected in parallel to the resistors. This will help us accurately measure the desired values.

Let's calculate I . Since the main current has not yet been distributed, I is equal to the current provided by the source.

$$I = 10 \text{ mA}$$

The equivalent resistance with respect to the terminals $a - b$ is $330 \parallel (220 + (220 \parallel (100 + 120))) = 330 \parallel 330$. From the current divider, we may calculate I_1 .

$$I_1 = 10 \cdot 10^{-3} \cdot \frac{330}{330 + 330} = 5 \text{ mA}$$

From here $I_2 = 5 \text{ mA}$. From the current divider, we may also calculate I_3 .

$$I_3 = 5 \cdot 10^{-3} \cdot \frac{220}{220 + 100 + 120} = 2.5 \text{ mA}$$

Therefore, $I_4 = 2.5 \text{ mA}$.

We may now use Ohm's Law to calculate the voltages across the resistors.

$$V_1 = 330 \cdot 5 \cdot 10^{-3} = 1.65 \text{ V}, \quad V_2 = 220 \cdot 5 \cdot 10^{-3} = 1.1 \text{ V}, \quad V_3 = 220 \cdot 2.5 \cdot 10^{-3} = 0.55 \text{ V}$$

$$V_4 = 100 \cdot 2.5 \cdot 10^{-3} = 0.25 \text{ V}, \quad V_5 = 120 \cdot 2.5 \cdot 10^{-3} = 0.3 \text{ V},$$

$I = 10 \text{ mA}, \quad I_1 = 5 \text{ mA}, \quad I_2 = 5 \text{ mA}, \quad I_3 = 2.5 \text{ mA}, \quad I_4 = 2.5 \text{ mA}$ $V_1 = 1.65 \text{ V}, \quad V_2 = 1.1 \text{ V}, \quad V_3 = 0.55 \text{ V}, \quad V_4 = 0.25 \text{ V}, \quad V_5 = 0.3 \text{ V}$

3.2 Find the equivalent resistance R_{ab} between points a and b for the circuit in *Figure 7*.


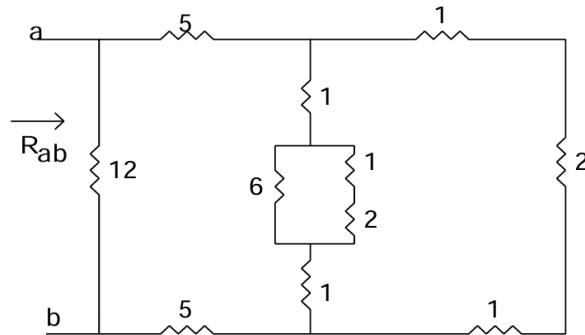


Figure 7.


Answer: Recall that R_{eq} is equal to the sum of the resistance of the resistors connected in series. R_{eq} is equal to the reciprocal of the sum of the reciprocal of each resistance of the resistors connected in parallel. In mathematical notation:

$$R_{eq,s} = \sum_{i=1}^n R_i = R_1 + R_2 + \dots + R_n \quad \frac{1}{R_{eq,p}} = \sum_{i=1}^n \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

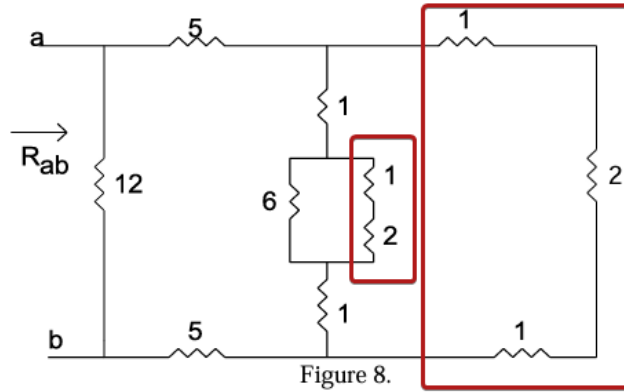
We approach this question by reducing the number of resistors to obtain an equivalent circuit with respect to the terminals a and b .



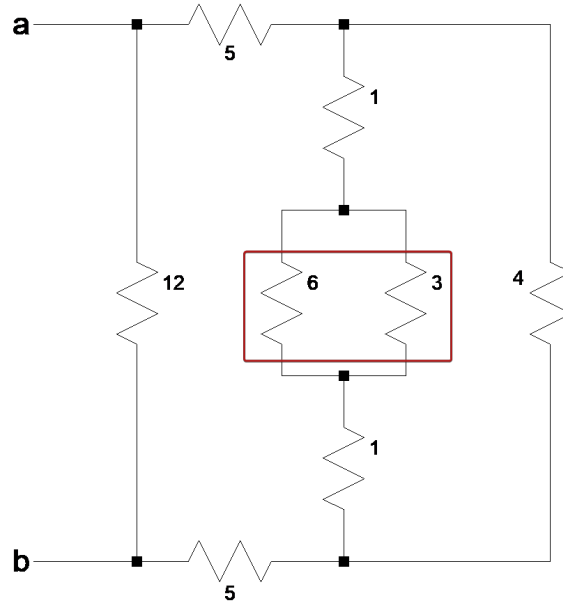
$$R_{eq, left} = 1 + 2 = 3\Omega \quad R_{eq, right} = 1 + 2 + 1 = 4\Omega$$



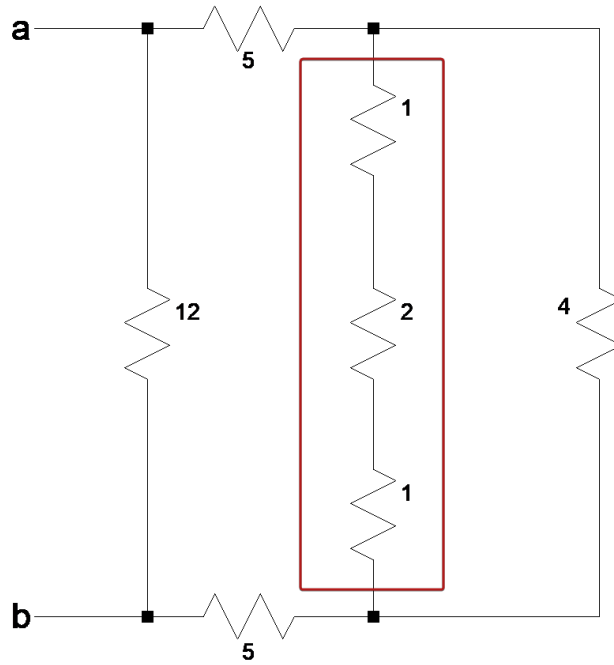
$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3} \Rightarrow R_{eq} = 2\Omega$$




$$R_{eq} = 1 + 2 + 1 = 4 \, \Omega$$

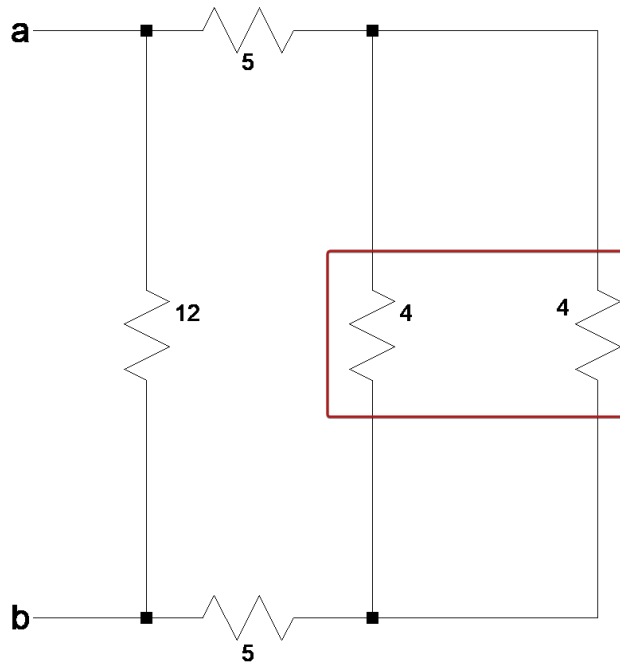

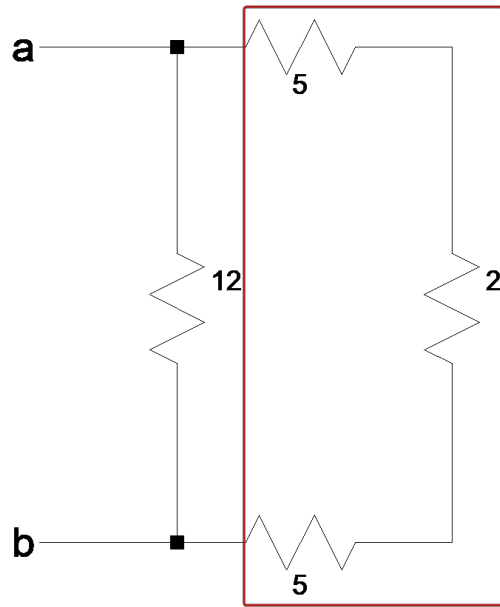
$$\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{4} \implies R_{eq} = 2 \, \Omega$$



$$R_{eq} = 5 + 2 + 5 = 12 \, \Omega$$

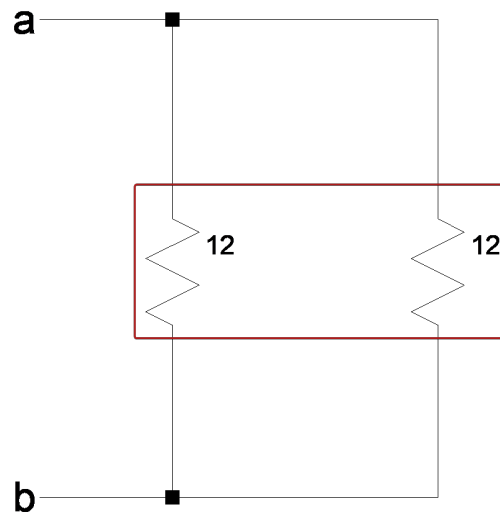
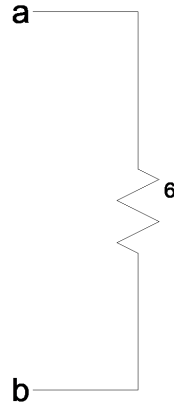
$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{12} \Rightarrow R_{eq} = 6 \, \Omega$$



Therefore, we conclude that $R_{ab} = 6 \Omega$.

3.3 Figure 10 shows a carbon resistor. For each of the resistance values given, write down the correct color bands.

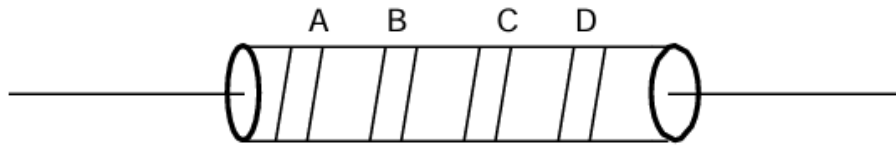


Figure 10.

- a) $100 \pm 10\%$ b) $120 \pm 5\%$ c) $220 \pm 20\%$ d) $330 \pm 10\%$

Answer: Looking up the color chart, the color bands are given below.

Option\Band	A	B	C	D
a)	Brown	Black	Brown	Silver
b)	Brown	Red	Brown	Gold
c)	Red	Red	Brown	None
d)	Orange	Orange	Brown	Silver

3.4 For the circuit given in Figure 9, find the Thévenin and Norton equivalent circuits with respect to terminals a and b .


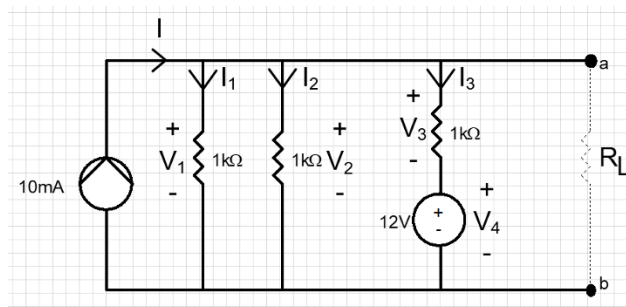


Figure 9.

Answer: Zero the sources, then we get

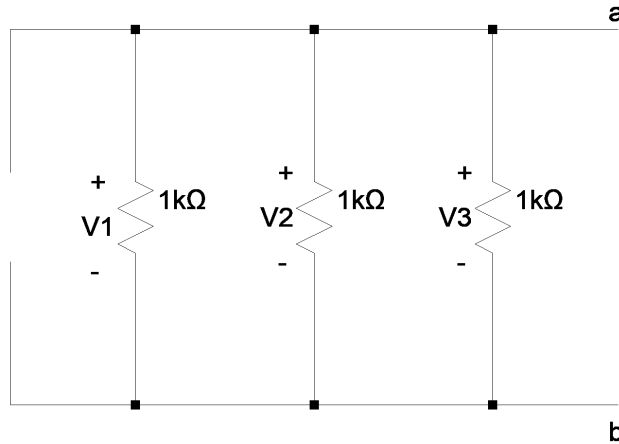


$$R_{th} = R_{ab} = (1k) \parallel (1k) \parallel (1k) = \frac{1000}{3} \Omega$$

Analyze the open circuit and find V_{th} . Apply the node voltage method by choosing b as the ground.

$$-10 \text{ m} + \frac{V_a}{1 \text{ k}} + \frac{V_a}{1 \text{ k}} + \frac{V_a - 12}{1 \text{ k}} = 0 \implies V_a = \frac{22}{3} \text{ V}$$

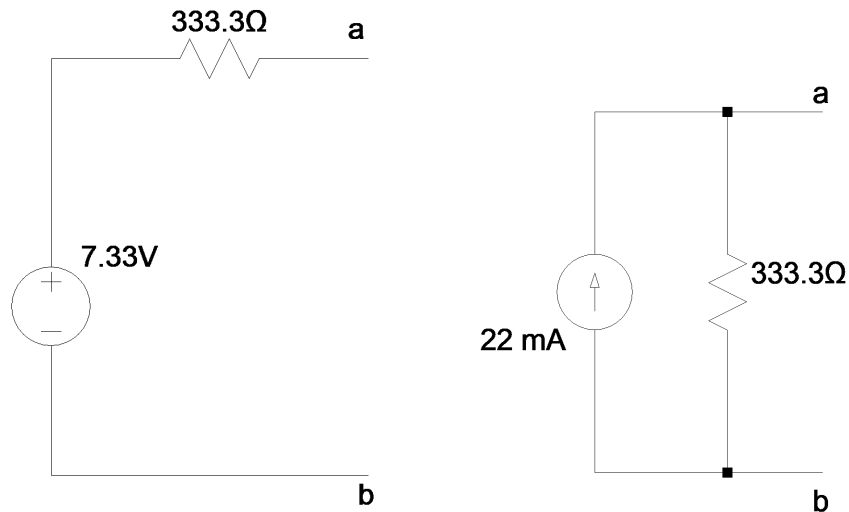Therefore, $V_{th} = V_a - 0 = \frac{22}{3} \text{ V}$. We obtain the Norton-equivalent circuit by $I_{sc} = \frac{V_{th}}{R_{th}} = \frac{\frac{22}{3}}{\frac{1000}{3}} = \frac{11}{500} \text{ A} = 22 \text{ mA}$. The Thévenin- and Norton-equivalent circuits are as follows, respectively.



3.5 Using the superposition principle, find V_{ab} given in *Figure 10*.

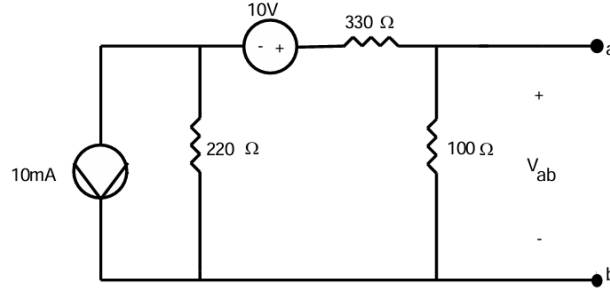


Figure 10.

Answer: First, deactivate 10 V source, i.e., replace it with a short circuit. Assign a node-voltage label to the top-left node, say V_c . Then

$$10 \text{ m} + \frac{V_c}{220} + \frac{V_c}{330 + 100} = 0 \implies V_c = -1.45 \text{ V}$$

The voltage across 100Ω is $100 \cdot \frac{-1.45}{330 + 100} = -0.34 \text{ V}$

Deactivate the current source, i.e., replace it with an open circuit. Let I be the circulating current. Applying KVL, we get

$$220I - 10 + 330I + 100I = 0 \implies I = \frac{1}{65} \text{ A}$$

The voltage across the resistor becomes $100 \cdot \frac{1}{65} = 1.54 \text{ V}$

Using the superposition principle, we sum up the values algebraically. Therefore,

$$\boxed{V_{ab} = -0.34 + 1.54 = 1.2 \text{ V}}$$

3.6 For the circuit given in *Figure 9*, find the dissipated and generated powers.

Answer: We have the Thévenin voltage from 3.4.

$$I_1 = \frac{V_{th}}{1 \text{ k}\Omega} = 7.33 \text{ mA}, \quad I_2 = \frac{V_{th}}{1 \text{ k}\Omega} = 7.33 \text{ mA}, \quad I_3 = \frac{V_{th} - 12}{1 \text{ k}\Omega} = -4.67 \text{ mA}$$

$$\boxed{P_{10 \text{ mA}} = -I \cdot V_{10 \text{ mA}} = 10 \text{ m} \cdot 7.33 = -73.3 \text{ mW}, \quad P_{1000 \Omega} = \frac{V_1^2}{1000} = \frac{(7.33)^2}{1000} = 53.7 \text{ mW}}$$

$$\boxed{P_{1000 \Omega} = \frac{V_2^2}{1000} = \frac{(7.33)^2}{1000} = 53.7 \text{ mW}, \quad P_{1000 \Omega} = \frac{(V_{th} - 12)^2}{1000} = \frac{(-4.67)^2}{1000} = 21.8 \text{ mW}}$$

$$\boxed{P_{12 \text{ V}} = (-4.67 \text{ m})(12) = -56.0 \text{ mW}}$$

3.7 Show that the total power generated by the sources in *Figure 9* is equal to the total power dissipated by the resistors.

Answer: The small error is due to the approximations based on the power values.

$$P_{dis} = 53.7 + 53.7 + 21.8 = 129.2 \text{ mW}, \quad P_{gen} = -73.3 - 56.0 = -129.3 \text{ mW}$$

$$|129.2 \text{ mW}| \approx |-129.3 \text{ mW}| \implies \sum |P_{dis}| = \sum |P_{gen}|$$

3.8 Determine the value of R_L that is to be connected between a and b to realize the maximum power transfer.

Answer: Set $R_L = R_{th}$ to obtain maximum power transfer to R_L . This comes from the fact that when we write a power function for R_L and take the derivative with respect to R_L , we notice that $R_L = R_{th}$ gives rise to a maximum. Therefore, $\boxed{R_L = 333.3 \Omega}$.